

Resistor	value	equivalent circuit	error ± %
Rref1-1	10k	10k	0
R 1-1-1	5471.9	$((1.0000\text{ k}\Omega + 27.0000\text{ k}\Omega) \parallel 6.8000\text{ k}\Omega)$	735.632 mΩ (0.013444%)
R 1-1-2	5461.6	$(560\text{ }\Omega + (1.0000\text{ k}\Omega + 3.9000\text{ k}\Omega))$	1.6 Ω (0.029295%)
R 1-1-3	5460.2	$(560\text{ }\Omega + (1.0000\text{ k}\Omega + 3.9000\text{ k}\Omega))$	200.000 mΩ (0.003663%)
R 1-1-4	52205	$(470\text{ }\Omega + (4.7000\text{ k}\Omega + 47.0000\text{ k}\Omega))$	35 Ω (0.067043%)
R 1-1-5	5469.1	$(470\text{ }\Omega + (10.0000\text{ k}\Omega \parallel 10.0000\text{ k}\Omega))$	900.000 mΩ (0.016456%)
Rof 1-1	6284.9	$(3.3000\text{ k}\Omega + (4.7000\text{ k}\Omega \parallel 8.2000\text{ k}\Omega))$	2.6969 Ω (0.042911%)
Rref1-2	10k	10k	0
R 1-2-1	4437.5	$(390\text{ }\Omega + (6.8000\text{ k}\Omega \parallel 10.0000\text{ k}\Omega))$	119.048 mΩ (0.002683%)
R 1-2-2	4437.5	$(390\text{ }\Omega + (6.8000\text{ k}\Omega \parallel 10.0000\text{ k}\Omega))$	119.048 mΩ (0.002683%)
R 1-2-3	4437.5	$(390\text{ }\Omega + (6.8000\text{ k}\Omega \parallel 10.0000\text{ k}\Omega))$	119.048 mΩ (0.002683%)
R 1-2-4	4437.5	$(390\text{ }\Omega + (6.8000\text{ k}\Omega \parallel 10.0000\text{ k}\Omega))$	119.048 mΩ (0.002683%)
R 1-2-5	4437.5	$(390\text{ }\Omega + (6.8000\text{ k}\Omega \parallel 10.0000\text{ k}\Omega))$	119.048 mΩ (0.002683%)
Rof 1-2	2531.2	$((3.3000\text{ k}\Omega + 3.9000\text{ k}\Omega) \parallel 3.9000\text{ k}\Omega)$	1.4703 Ω (0.058086%)
Rref2-1	10k	10k	0
R 2-1-1	2985.4	$((2.7000\text{ k}\Omega + 10.0000\text{ k}\Omega) \parallel 3.9000\text{ k}\Omega)$	1.6651 Ω (0.055773%)
R 2-1-2	1231.3	$((470\text{ }\Omega \parallel 3.3000\text{ k}\Omega) + 820\text{ }\Omega)$	105.836 mΩ (0.008595%)
Rof 2-1	5885.6	$((4.7000\text{ k}\Omega + 39.0000\text{ k}\Omega) \parallel 6.8000\text{ k}\Omega)$	1.2436 Ω (0.021129%)
Rref2-2	10k	10k	0
R 2-2-1	2028.4	$((270\text{ }\Omega + 3.3000\text{ k}\Omega) \parallel 4.7000\text{ k}\Omega)$	499.637 mΩ (0.024632%)
R 2-2-2	7653.9	$((680\text{ }\Omega + 10.0000\text{ k}\Omega) \parallel 27.0000\text{ k}\Omega)$	1.0338 Ω (0.013506%)
Rof 2-2	8583	$((390\text{ }\Omega \parallel 27.0000\text{ k}\Omega) + 8.2000\text{ k}\Omega)$	1.4469 Ω (0.016857%)
Rref2-3	10k	10k	0
R 2-3-1	2856.6	$((680\text{ }\Omega + 10.0000\text{ k}\Omega) \parallel 3.9000\text{ k}\Omega)$	190.123 mΩ (0.006656%)
R 2-3-2	40771	$((3.3000\text{ k}\Omega \parallel 3.9000\text{ k}\Omega) + 39.0000\text{ k}\Omega)$	16.5 Ω (0.040470%)
Rof 2-3	7694	$((1.0000\text{ k}\Omega + 8.2000\text{ k}\Omega) \parallel 47.0000\text{ k}\Omega)$	49.822 mΩ (0.000648%)
Rref2-4	10k	10k	0
R 2-4-1	3910.7	$(390\text{ }\Omega + (820\text{ }\Omega + 2.7000\text{ k}\Omega))$	700.000 mΩ (0.017900%)
R 2-4-2	6964.6	$((330\text{ }\Omega \parallel 330\text{ }\Omega) + 6.8000\text{ k}\Omega)$	400.000 mΩ (0.005743%)
Rof 2-4	1738.6	$((820\text{ }\Omega + 1.0000\text{ k}\Omega) \parallel 39.0000\text{ k}\Omega)$	253.503 mΩ (0.014581%)